

Aryan College

Analog Circuit and Communication

Unit I:

Power Supply and Filters

1. Give diagram of a regulated power supply and name each component? [2017]
2. What is principle of SMPS? [2017,2014]
3. Draw the circuit diagram of half-wave rectifier? [2017]
4. Draw circuit diagram of L-section filter? [2017]
5. Draw the circuit diagram of bridge rectifier and explain its working? [2017]
6. Draw circuit diagram of full wave rectifier and explain its working? Derive expression for its efficiency and ripple factor? [2017]
7. Draw circuit diagram for a π -section filter and explain its working. Derive expression for ripple factor and explain its dependency on load resistance? [2017]
8. Define ripple factor? [2016]
9. Define bandwidth of an amplifier? [2016]
10. Define noise? [2016,2015]
11. Draw the circuit diagram of a bridge rectifier? [2016]
12. Draw the circuit diagram of logarithmic amplifier? [2016]
13. Draw the block diagram of regulated power supply. Explain the principle and working of a switch mode supply? [2016]
14. Draw a circuit of full-wave rectifier? [2015]
15. Define rectification efficiency? [2015]
16. Explain bridge rectifier, draw suitable diagram and wave form? [2015,2013]
17. What is filter and explain all types of filters with circuit diagram? [2015]
18. Write a note on principle and working of SMPS? [2015]
19. What is bridge rectifier? [2014]
20. Draw block diagram of regulated power supply? [2014]
21. What is Full wave Rectifier? Obtain expression for its efficiency, Ripple factor and Regulation? [2014]
22. What is value of ripple factor for half wave and full wave rectifier? [2013]
23. What is role of SMPS? [2014,2013]

Unit II:

RC Coupled Amplifier and Feedback

1. What do you mean by feedback? Draw a basic feedback circuit? [2017,2014]
2. What is negative feedback? Explain how negative feedback improves bandwidth? [2017]
3. Explain working of a single stage RC coupled CE amplifier with help of circuit diagram? Analyze its frequency response for mid frequency range? [2017]
4. Define negative feedback? [2016]
5. Define slew rate? [2016]
6. Write an equation to explain the effect of negative feedback on bandwidth of an amplifier? [2016]
7. Draw the circuit diagram of R-C coupled amplifier? [2016]
8. Compare the effect of positive and negative feedback on:- [2016,2014]
 - a) Gain
 - b) Bandwidth

Aryan College

- c) Noise
- d) Input Impedance of an amplifier
- e) Output impedance of an amplifier
- 8. What is R.C. Coupled amplifier? Give analysis and frequency response of single stage RC coupled CE Amplifier? [2014,2013]
- 9. What is an Amplifier? [2014]
- 10. Design a feedback network for an non-inverting amplifier. The voltage gain of the feedback network is $(1/22)$? [2013]
- 11. Write two differences between series and shunt regulator? [2013]
- 12. Explain the effect of negative feedback on the input impedance of voltage shunt? [2013]
- 13. When two diodes are connected back to back with two N-sides is joint together. Can it become a transistor? [2013]
- 14. Draw electrical circuit model for the double ended differential amplifiers? [2013]
- 15. Define input bias current, input offset current, input and output offset voltage slew rate? [2013]

Unit III:

Operational Amplifiers

- 1. Define offset voltage for OP-AMP? [2017]
- 2. Explain virtual ground for OP-AMP? [2017]
- 3. Define voltage gain of an amplifier in dB unit? [2017]
- 4. Write five characteristics of an ideal OP_AMP? [2017]
- 5. Explain the pin diagram of an OP-AMP. Evaluate expression for voltage gain for an inverting amplifier? [2017]
- 6. Draw circuit diagram of a summing amplifier (adder) using OP-AMP and explain its working? [2017,2014]
- 7. Draw a diagram of a differentiator circuit? [2016]
- 8. Draw a diagram to show a triangular and square wave? [2016]
- 9. What is common mode rejection ratio? Explain. [2016,2014]
- 10. Define degree of differential equation? [2015]
- 11. Define Oscillator? [2015]
- 12. Explain monostable multi-vibrate? [2015]
- 13. Explain multi-vibrator in detail. Differentiate between oscillators a multi-vibrate? [2015]
- 14. Explain any three OP-Amp applications in detail? [2015]
- 15. Explain parameters of OP-Amp? [2015]
- 16. Define linear voltage regulation? [2015]
- 17. Write short note on :- [2016]
 - a) Frequency response of operational amplifier?
 - b) Voltage follower?
 - c) Amplitude modulation
 - d) Advantages of frequency modulation
 - e) Choke input filter
 - f) Comparator
 - g) Monostable multivibrator
- 18. Discuss basic operational amplifier's following uses as:- [2016]
 - a) Integrator
 - b) Series regulators
- 19. Define Square Law Diode modulator? [2014]
- 20. What is square wave (a stable) Generator? [2014]

Aryan College

21. What is triangular wave Generator? [2014]
22. What is three terminal regulator? [2014]
23. What is offset voltage? [2014]
24. Define the slew rate (SR) of an op-Amp? [2013]
25. A wein bridge oscillator is used for operate at $F_0 = 10\text{KHz}$. If the value of R is $100\text{K}\Omega$, find the value of the capacitor of the capacitor C? [2013]
26. Explain the use of op-Amp when it is used as : [2013]
 - i. Voltage follower
 - ii. Summer
27. How to generate the amplitude modulate wave with the help of square law diode modulator? [2013]
28. Describe the working of a comparator along with the suitable schematic diagram? [2013]
29. What is multi-vibrator? Explain the operation of monostable multi-vibrator and draw the o/p voltage wave-form? [2013]

Unit IV:

Communication

1. What do you mean by demodulation? [2017,2016,2014]
2. Derive equation for frequency modulated wave? [2017]
3. Draw a diagram to explain the concept of frequency modulation? [2016]
4. What do you understand by phase modulation? Explain. [2016]
5. What do you understand by wave propagation? [2015]
6. The amplitude of AM signal is 5V and that of carrier wave 50. Calculate the percentage of modulation index? [2015]
7. Write any two advantages of modulation? [2015]
8. Explain demodulation of AM? [2015]
9. Define FM? [2015]
10. Discuss relation between PM and FM? [2015]
11. Explain modulation, its types and need? [2015,2014,2013]
12. Explain AM and FM radio receiver using block diagram approach? [2015,2014]
13. What do you mean by Frequency modulation? [2013]
14. Explain in brief the need of modulation? [2013]
15. Explain the difference between frequency and amplitude modulation? [2013]